

# ECE 210 Review

## Midterm Two Fall 2024

December 6, 2025

Created by HKN

---

### 1 [25 points] The three parts of this problem can be solved independently.

1. Determine the phasor of the sinusoidal signal

$$f(t) = 10 \sin \left( \frac{\pi}{4}t - \frac{3\pi}{4} \right).$$

Express it both in polar and rectangular. **(5 points)**

(a) Polar:

(b) Rectangular:

2. Determine the phasor of the sinusoidal signal

$$f(t) = 4 \cos \left( 5t + \frac{\pi}{4} \right) + 12 \cos \left( t + \frac{7\pi}{4} \right).$$

Express it in either polar or rectangular form. **(5 points)**

3. Given the LTI system with frequency response


$$H(\omega) = \frac{2}{12 + j\omega}$$

and the input

$$f(t) = 7 + \sin \left( 5t + \frac{\pi}{2} \right) + \cos \left( 12t + \frac{\pi}{4} \right),$$

determine the output  $y(t)$ . **(25 points)**

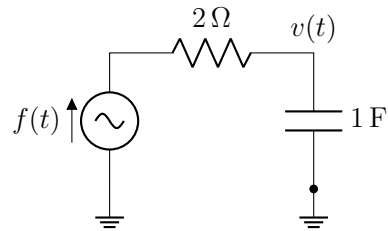**2 [15 points]** Consider the circuit shown below.



For  $t > 0$ , the source voltage is

$$f(t) = 4e^{-t}u(t) \text{ V},$$

and the capacitor has initial value  $v(0^-) = 1 \text{ V}$ .

1. Derive the differential equation (ODE) governing the capacitor voltage  $v(t)$  for  $t > 0$ .  
**(7 points)**

2. Solve for  $v(t)$  for  $t > 0$ , using the initial condition. **(8 points)**